



Figure 2. Dual Differential Amplifier with Current Mirror Biasing. Set Up for Testing of Differential and Common Mode Gain.