

Two Port Parameters

$$\begin{bmatrix} v_2 \\ i_2 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} + \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} \quad (\text{abcd, or chain parameters})$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad (\text{z parameters})$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad (\text{y parameters})$$

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} \quad (\text{h parameters})$$

$I_1, I_2, V_1,$ and V_2 are independent sources within the two port network.

$$a = \left. \frac{v_2 - V_2}{v_1} \right|_{i_1 = 0} \quad (\text{dimensionless})$$

$$b = \left. \frac{v_2 - V_2}{i_1} \right|_{v_1 = 0} \quad (\text{ohms})$$

$$c = \left. \frac{i_2 - I_2}{v_1} \right|_{i_1 = 0} \quad (\text{siemens})$$

$$d = \left. \frac{i_2 - I_2}{i_1} \right|_{v_1 = 0} \quad (\text{dimensionless})$$

$$\left. \begin{array}{l} V_2 = v_2 \\ i_1 = 0 \end{array} \right|_{v_1 = 0} \quad \mathbf{V}$$

$$\left. \begin{array}{l} I_2 = i_2 \\ v_1 = 0 \end{array} \right|_{i_1 = 0} \quad \mathbf{A}$$


If I_1 and I_2 (independent sources) are zero the value of the y parameters can be calculated using:

$$y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$$

$$y_{21} = \frac{i_2}{v_1} \Big|_{v_2=0}$$

$$y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0}$$

$$y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$

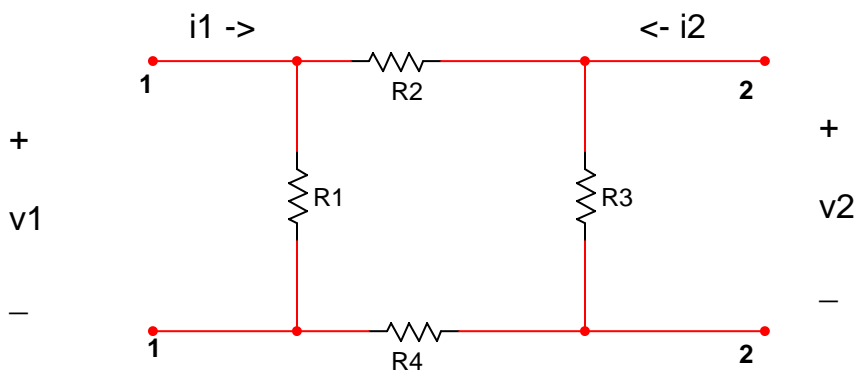


$$y_{12} = -\frac{1}{R_2 + R_4}$$

$$y_{22} = \frac{1}{R_3 \parallel (R_2 + R_4)}$$

$$y_{21} = -\frac{1}{R_2 + R_4}$$

$$y_{11} = \frac{1}{R_1 \parallel (R_2 + R_4)}$$

H Parameters for the BJT

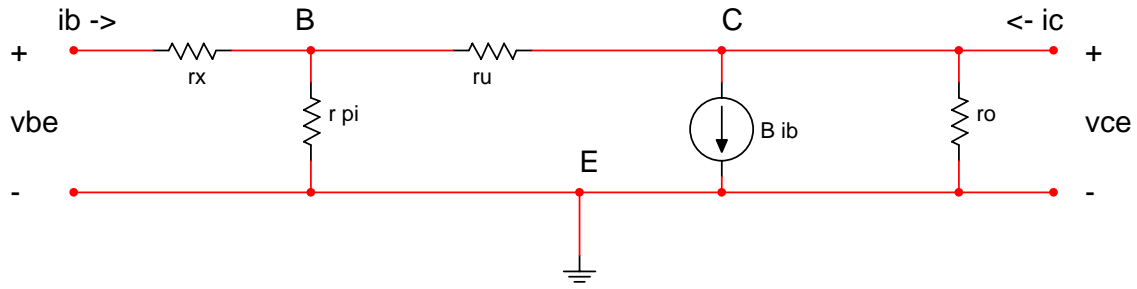

$$\begin{bmatrix} v_{be} \\ i_c \end{bmatrix} = \begin{bmatrix} h_{ie} & h_{re} \\ h_{fe} & h_{oe} \end{bmatrix} \begin{bmatrix} i_b \\ v_{ce} \end{bmatrix}$$

$$\begin{aligned} v_{be} &= h_{ie} i_b + h_{re} v_{ce} \\ i_c &= h_{fe} i_b + h_{oe} v_{ce} \end{aligned}$$

$$h_{ie} = \left. \frac{v_{be}}{i_b} \right|_{v_{ce}=0}$$

$$h_{re} = \left. \frac{v_{be}}{v_{ce}} \right|_{i_b=0}$$

$$h_{fe} = \left. \frac{i_c}{i_b} \right|_{v_{ce}=0}$$

$$h_{oe} = \left. \frac{i_c}{v_{ce}} \right|_{i_b=0}$$

$$\begin{bmatrix} v_{be} \\ i_c \end{bmatrix} = \begin{bmatrix} (r_x + r_{pi} \parallel r_u) & \left(\frac{r_{pi}}{r_u + r_{pi}} \right) \\ B & \left(\frac{1}{r_o} \right) \end{bmatrix} \begin{bmatrix} i_b \\ v_{ce} \end{bmatrix}$$